



**Hochschule
Augsburg** University of
Applied Sciences

Random Data Symbol Generator

VLSI/COMM Miniproject - Report

J Gibson, A Wiedholz

SS2021

Contents

1	Introduction	5
2	Background	6
3	Features	7
4	General Description	8
5	Design Description	9
6	Verification	11
6.1	Verification in simulation	11
6.2	Verification with MATLAB	12
7	Application Note	15
8	Appendix	15
8.1	References	15
8.2	Project Hierarchy	15
8.2.1	Module Hierarchy for Verification	15
8.2.2	Prototype Environment	15
8.3	VHDL Sources	15

List of Tables

1	Symbol generator - Description of I/O Signals	8
---	---	---

List of Figures

1	Overview of completed application	5
2	Overview PAM transmitter	5
3	BPSK symbol decision	6
4	Fibonacci lfsr	7
5	Entity description	8
6	Symbol generation	9
7	Timing diagram valid_o	10
8	Generation of the restart signal	10
9	LFSR1 with 6 Flip Flops	11
10	Verification of valid signal	11
11	Verification of restart signal	12
12	Correlation between the signals produced with first lfsr	14
13	Verification with python script	15

1 Introduction

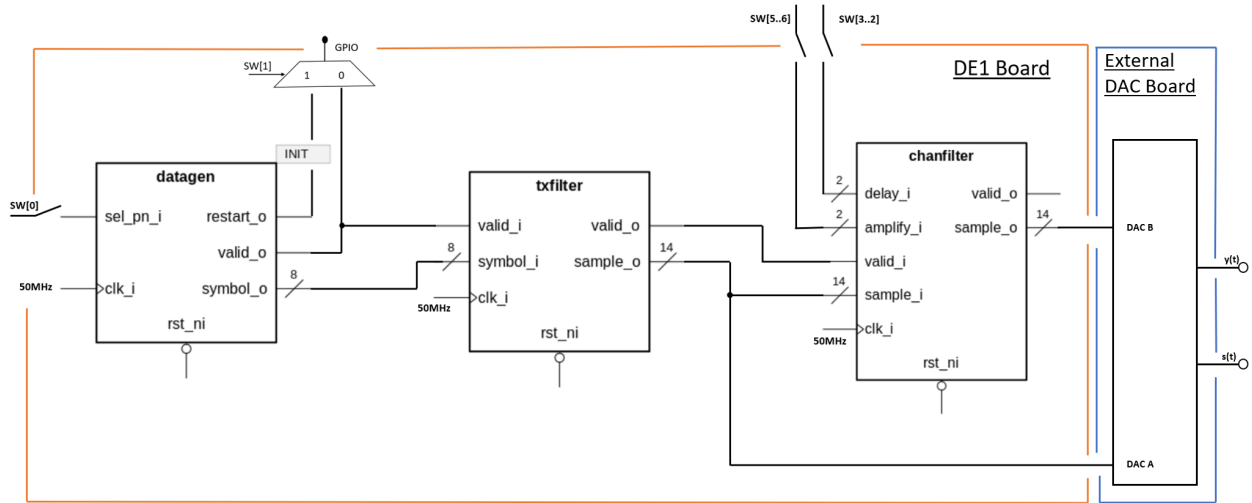


Figure 1: Overview of completed application

This report describes one of three subprojects which together are combined into one large application as shown in Figure 1. The overall application is a PAM-transmitter connected with a simulated channel filter. The PAM-transmitter can be seen in Figure 2 and the mentioned Channel Filter shall be applied to the signal $s(t)$. This system runs on an FPGA board that uses a default clock of 50MHz. The PAM-transmitter, comprising both Symbol Generator and Transmit Filter forms the basis of two of the three subprojects, with a Channel Filter providing the basis for the third. The symbol generator, with a symbol rate defined in the project specification which is eight times slower than the system clock, provides a new symbol with a rate of 6.25 MHz. The generated data are used by the Transmit Filter initially by upsampling the symbol stream by a factor of L and then filtering, resulting in the sample rate. This process can be done collectively using a Polyphase FIR filter (Mini Project 2). The channel filter (Mini Project 3) basically is a comb filter that has a variable delay and amplification. In this project the first component of the PAM-transmitter, the symbol generator, is implemented. As shown in Figure 2 the symbol generator basically consists of a bit source and a bit-to-symbol-mapper.

 


Figure 2: Overview PAM transmitter

In an ideal world each symbol produced by a symbol generator would be entirely arbitrary and so each symbol produced would have no correlation to the last. As we cannot simulate ideal

world conditions, it is necessary to use two different pseudo-random sequences for the Symbol Generator which shall be chosen by the user.

2 Background

The symbol generator in figure 2 basically consists of a bit generation (bit source) and a symbol decision (bit-to-symbol mapper). The bit source is taken from one of two possible Linear Feedback Shift Registers (LFSRs), which create a pseudo-random collection of bits. These bits are then mapped to either +1 or -1 for bits 0 and 1 respectively. Basically, this mapping can be compared with a Binary Phase Shifting Key (BPSK). BPSK is a two-phase modulation scheme where two bits (0 and 1) are represented as two different phase states on a constellation as shown in Figure 3 (in this case, +1 and -1).

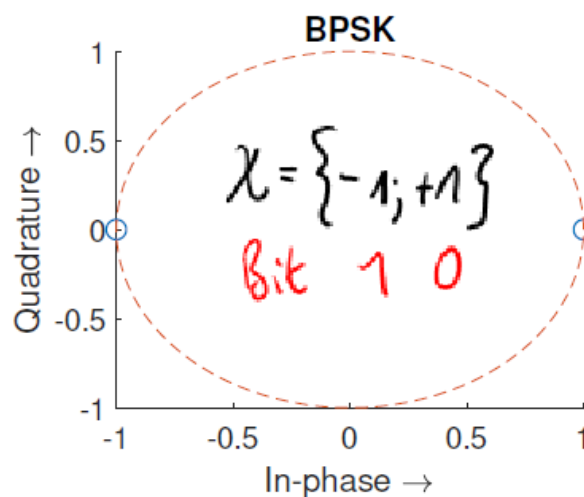


Figure 3: BPSK symbol decision

The symbol generator in this project produces a string of symbols that are not fully randomized. However, a series of pseudo-random symbols can be produced using a Fibonacci LFSR which repeats itself after a certain number of symbols (defined by the length of the LFSR). For example, if the size of the LFSR contains m flip-flops, then the resulting maximum length of the sequence is $2^m - 1$.

 


Figure 4: Fibonacci lfsr

The Fibonacci LFSR uses a shift register of a certain length, sets an initial condition to each Flip-Flop and creates feedback from one end to the other. With an initial condition we can set some of these Flip Flops to 0 and others to 1 while resetting the system. The feedback can be as simple as feeding the signal from one end to the other. Alternatively, it can be created with XOR gates which are fed by other signals of the LFSR. In the above example, the XOR gates get their inputs from FF 11, 13, 14, and 16. The inputs that are combined in the XOR gates can be described in a mathematical polynomial. For this example the equation would be $z^{16} + z^{14} + z^{13} + z^{11} + 1$. The 1 in this equation does not represent a source for an XOR gate; instead, it tells that the output of the XOR gates is fed to the first bit of the register.

As mentioned in Section 1 the generated symbols should be entirely arbitrary. If you calculate the correlation between these symbols it should create a perfect Dirac impulse. However, as a perfectly random string of symbols is impossible to implement practically, we must endure some level of correlation in our symbol stream. We can calculate this correlation and plot the result with MATLAB which shall be discussed further in section 6.2.

3 Features

The Random Signal Data Symbol Generator produces random symbols (+1 and -1) with a frequency of 6.25 MHz for a transmitter. Unfortunately, it is not possible to produce a perfect random string of symbols. However, an acceptable level of randomness can be obtained using a pseudo-random symbol generator. An LFSR with a specific length can produce a set number of pseudo-random sequences before repeating itself. As defined in the project specification, this task requires two separate sequence lengths of either $2^6 - 1$ or $2^{24} - 1$.

A user input allows one to switch between the different sequences provided by the two shift registers. To show at which point of time a new valid symbol can be sampled, a valid signal is produced. Additionally, a restart signal is created to indicate when the currently selected

sequence repeats itself. The user can produce many different series of symbols by setting the initial conditions differently.

4 General Description

The content of this project can be broken down into 2 main parts. Firstly, to create a symbol generator in MATLAB which generates a list of pseudo-random bits, maps them to the correct symbols and stores this list for later confirmation. MATLAB should also be used to generate an correlation diagram to show the level of randomness of the final symbol stream. The second part of the project involves implementing the symbol generator using VHDL and comparing the results to those produced in MATLAB. If both strings of data produced are the same, then it can be assumed that we have a working system.

The entity of the symbol generator that is implemented in VHDL is shown in Figure 5 below. An input signal is taken as sel_pn_i, and three outputs as restart_o, valid_o and symbol_o.

 


Figure 5: Entity description

Table 1: Symbol generator - Description of I/O Signals

Name	Type	Direction	Polarity	Description
clk_i	std_ulogic	IN	HIGH	clock
rst_ni	std_ulogic	IN	LOW	reset
sel_pn_i	std_ulogic	IN	HIGH	select lfsr
restart_o	std_ulogic	OUT	HIGH	sequence repeat
valid_o	std_ulogic	OUT	HIGH	symbol is valid

Name	Type	Direction	Polarity	Description
symbol_o	std_ulogic_vector	OUT	HIGH	symbol

5 Design Description

In general, the design idea of the symbol generator can be seen in Figures 6 and 8.

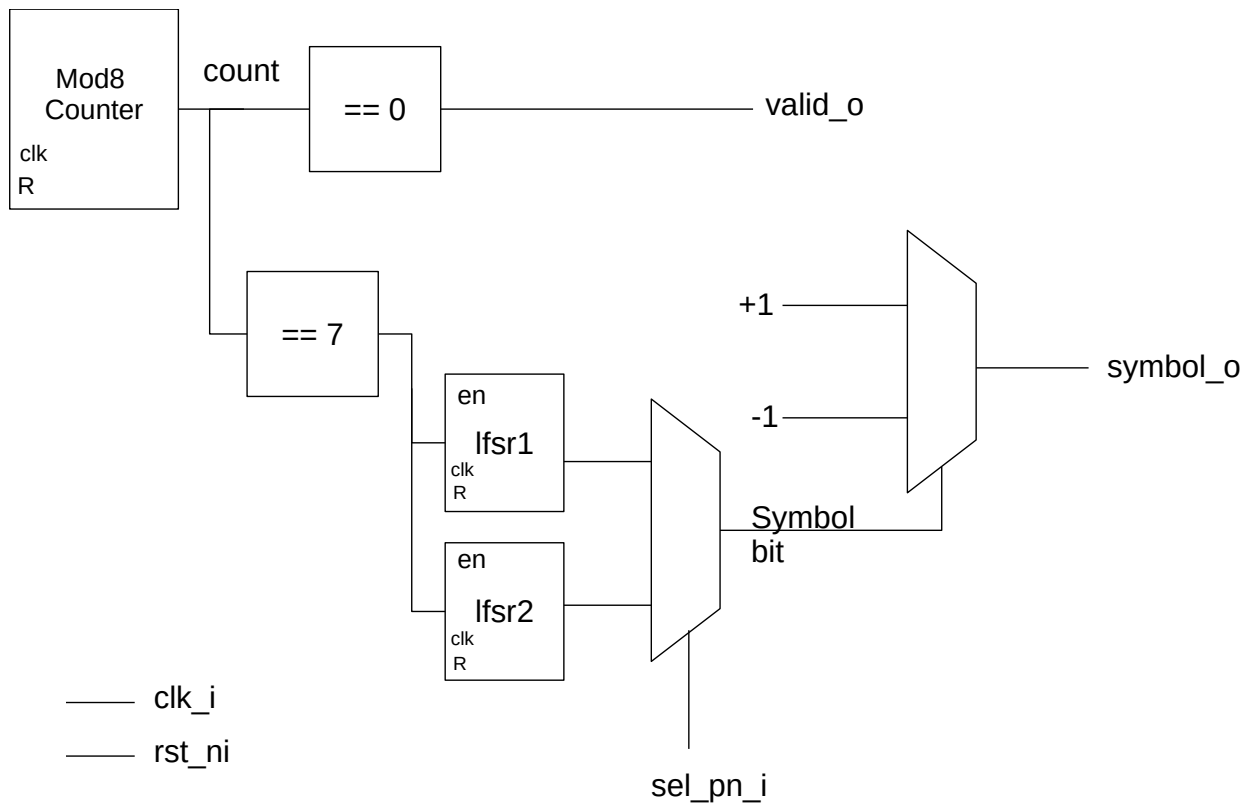


Figure 6: Symbol generation

Figure 6 shows a basic block diagram of the Symbol Generator. The output `symbol_o` of the model contains the desired symbol of the system depending on the value generated by the LFSR. The Mod8 counter counts from 0 to 7 in 8 clock cycles. On the 8th clock cycle the shift registers will be shifted. One clock cycle later, that is, at the first clock cycle of the new symbol, the `valid_o` signal outputs a 1. This scales the clock to a frequency of 6.25 MHz (i.e. 8 times slower than the default FPGA clock). This description of the `valid_o` signal leads to the timing diagram shown in Figure 7.

 


Figure 7: Timing diagram valid_o

As can be seen in the diagram above, the symbol is stable for 8 clock cycles and the valid signal is turned on for 1 clock cycle as soon as the new symbol is produced. This process effectively reduces the symbol rate to one eighth of the default clock frequency.

The shift register to be used as a symbol bit for the mapping can be chosen with sel_pn_i as the selector. The shift register that is chosen may be configured to a user input later (e.g. a key or switch on the FPGA board). The final symbol_o is determined by the output of a multiplexer which has a switching condition of the symbol bit. This changes the selected value to either +1 or -1 which is used as the input for the Polyphase FIR Filter in Mini-Project 2.

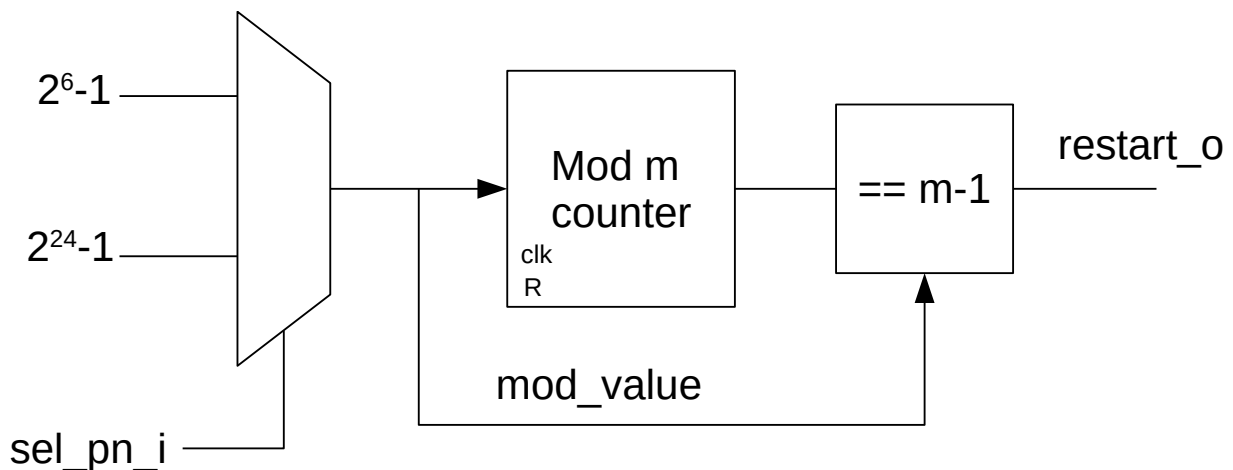


Figure 8: Generation of the restart signal

Figure 8 is another basic block diagram that shows how a programmable modulo counter can be used to generate the restart_o signal. This signal indicates the point at which the sequence of the currently selected shift register repeats itself. The 'm' in Figure 8 does not apply to the length of the shift register but represents the modulo_value so equals either $2^6 - 1$ or $2^{24} - 1$. The sel_pn_i signal selects the shift register to be used as the symbol bit and programs the modulo counter to compare the current counter value to the modulo_value - 1, thereby determining when the sequence of the selected shift register repeats.

Figure 9 below shows a representation of our Fibonacci LFSR that creates a sequence with a maximum length of $2^6 - 1$ symbols. The design of our LFSR differs from that displayed in Figure 4 as two Flip-Flops rather than four are used to act as an input to our XOR gate (Flip-Flops 5 and 6). The rightmost register is used as the output of the LFSR and is named symbol_bit, which can be seen in Figure 6.

 


Figure 9: LFSR1 with 6 Flip Flops

6 Verification

Two steps were used to verify our design. Firstly, in simulation with Modelsim, the basic functionality was tested. This means that periods of the valid_o signal and restart signal and the basic symbol generation are evaluated. Secondly, it was tested if a MATLAB generated symbol sequence can be reproduced from the VHDL design and calculated how random the produced sequence really is.

6.1 Verification in simulation

In the simulation the design was reset and run as long as was needed to produce the desired amount of symbols. With setting cursors in the generated waves it is possible to determine the frequency of the valid and the restart signal. The following snippet in Figure 10 from the simulation the period of the valid signal was measured:

 


Figure 10: Verification of valid signal

The period of the valid signal is 160 ns which means that the frequency is 6.25MHz according to $f = \frac{1}{T} = \frac{1}{160ns} = 6.25MHz$

It also tests if the restart signal is triggered at the correct frequency. For this, channel 0 is selected in the testbench which means that the LFSR with a maximum sequence length of $2^6 - 1 = 63$ is selected.

 


Figure 11: Verification of restart signal

The period of the signal is 10080 ns which results in 63 symbols according to $\frac{10080\text{ns}}{8 \cdot 20\text{ns}} = 63$. In this calculation $8 \cdot 20\text{ns}$ describes the symbol period.

6.2 Verification with MATLAB

In MATLAB it is possible to create a Fibonacci LFSR with the so called [PseudoNumber Generator](#). This is embedded in a script that produces a pseudo random symbol sequence with a certain length. This sequence can be written into a file that is then compared to a file that is written by a testbench for the VHDL design.

```
close all; clear *;

% Whether data shall be written to file or not
writeDataToFile = 1;

% use 2^6-1 or 2^24-1 as maximum sequence length
use_six = true;

% Create PN-sequence object with maximum-length sequence
lfsr = comm.PNSequence;
if use_six == true
    lfsr.Polynomial = [6 1 0];
    lfsr.InitialConditions = [1 1 0 0 0 0];
else
    lfsr.Polynomial = [24 1 0];
    ic = zeros(1,24,'uint32');
    ic(1) = 1;
    ic(2) = 1;
    lfsr.InitialConditions = ic;
end

% if you use second lfsr you should produce ~20000 samples per frame to get the desired
% correlation
lfsr.SamplesPerFrame = 500;

disp(['Initial state of LFSR: ' num2str(bin2dec(num2str(lfsr.InitialConditions))))];

% Create pseudo-random bit sequence
bits = lfsr();

% Bit-to-symbol mapping with w_out as symbol wordlength
w_out = 8;
symbols = []; % Requires your input
for i = 1:lfsr.SamplesPerFrame
```

```

    if bits(i) == 1
        symbols(i) = -1;
    else
        symbols(i) = 1;
    end
end

% Save output data to file to compare to VHDL-model (integer representation)
if writeDataToFile == 1
    save_variable(symbols, '%d', '../sim/datagen/log/datagen_result_ref.dat');
end

% Plot bit sequence
figure(1);
subplot(211);
stem(bits(1:10)); box off;
yticks([0 1]);
xlabel('Symbol index n \rightarrow'); ylabel('Bit \rightarrow');

% Autocorrelation
autocorr = dsp.Autocorrelator;
autocorr.MaximumLagSource = 'Property';
autocorr.MaximumLag = 50;
autocorr.Scaling = 'Biased';

% Calculate autocorrelation up to some lag
exx = autocorr(symbols'); % Requires your input

subplot(212);
stem(exx); box off; % Requires your input
xlabel('Lag i \rightarrow'); ylabel('E{x[n]x^{*}[n-i]} \rightarrow');

```

Autocorrelation is the correlation of a signal with a delayed copy of itself as a function of delay and so it is the similarity of a signal over a set period of lag. From Figure 12, we can observe two plots, the first is the symbol bit defined by the output of the first LFSR. In this case the first ten bits show {0,0,0,0,1,1,0,0,0,1}. The lower plot displays the autocorrelation of the signal. We see a Dirac puls at at lag of 1 and at the other lags a correlation nearly zero what means that our signal is already pretty random and uncorrelated. As some points lie very close to zero fluctuating about it slightly, we must assume that our signal is not perfectly random. Although a small level of correlation between the bits is produced by the LFSR it is acceptable for this application. The plots shown in Figure 12 are used to depict our first LFSR with a length of $2^6 - 1$ and we use a value of 500 symbols per frame to show this. To show our second LFSR correctly we must set the symbols per frame to a much higher value e.g. 20000 to avoid wrapping of the signal.

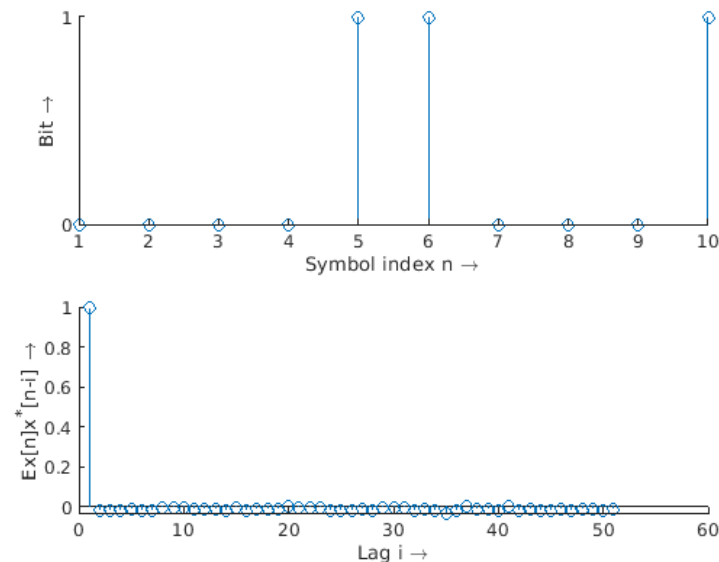


Figure 12: Correlation between the signals produced with first lfsr

If the file generated by MATLAB is the same as the one generated by the testbench in Modelsim then it will be possible to reproduce the symbol sequence from MATLAB in the VHDL design. With the following python script these two files were compared with each other. As our MATLAB script produces +1 and -1 for the symbols that equal 127 and -128 in the file that was written by the VHDL testbench, it is necessary to first convert the testbench generated file into the desired format.

```
import filecmp
from pathlib import Path

if __name__ == "__main__":
    matlab_file = "log/datagen_result_ref.dat"
    vhdl_file = "log/datagen_result.dat"
    with open(vhdl_file, "rt") as f:
        content = f.readlines()

    # matlab generates 1 and -1 as symbols so we have to replace 127 and -128 in our file
    # that was generated by testbench
    new_content = list()
    for line in content:
        if '127' in line:
            line = line.replace('127', '1')
        elif '128' in line:
            line = line.replace('-128', '-1')
        new_content.append(line)

    # write the new file
    with open(vhdl_file, "w") as f:
        for line in new_content:
            f.write(line)

    # check if the same amount of symbols was generated
    if Path(matlab_file).stat().st_size == Path(vhdl_file).stat().st_size:
        # check if the files are the same
        if filecmp.cmp(matlab_file, vhdl_file) is True:
            print("The files are the same")
```

```
else:
    print("The files are not the same")
else:
    print("The files do not have the same byte size, probably not the same amount of symbols
    ↳ generated")
```

7 Application Note

The following test environment on a DE1 prototype board uses a system clock frequency of 50 MHz. A prescaler is parameterised to generate an output signal with a period of 1 ms.

8 Appendix

 


Figure 13: Verification with python script

8.1 References

- [Wiki: Fibonacci Linear-feedback shift register](#)

8.2 Project Hierarchy

8.2.1 Module Hierarchy for Verification

```
t_datagen_fileio(tbench)
datagen_structure(rtl)
```

8.2.2 Prototype Environment

Produced by Prof. Dr.-Ing Matthias Kamuf

8.3 VHDL Sources

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY datagen IS
  GENERIC (
    INIT : integer);
  PORT (
    clk_i      : IN  std_ulogic;
    rst_ni     : IN  std_ulogic;
    sel_pn_i   : IN  std_ulogic;
    restart_o  : OUT std_ulogic;
    valid_o    : OUT std_ulogic;
    symbol_o   : OUT std_ulogic_vector(7 DOWNTO 0));
END datagen;

ARCHITECTURE structure OF datagen IS

  CONSTANT PLUS1  : integer := 2**(symbol_o'length-1)-1;
  CONSTANT MINUS1 : integer := -2**(symbol_o'length-1);

  CONSTANT SR1_LENGTH : integer := 6;
  CONSTANT SR2_LENGTH : integer := 24;

  CONSTANT MOD_COUNTER1 : integer := 2**SR1_LENGTH -1;
  CONSTANT MOD_COUNTER2 : integer := 2**SR2_LENGTH -1;

  -- counter for valid_o signal
  SIGNAL current_state_mod8_counter, next_state_mod8_counter: unsigned(2 DOWNTO 0);

  -- enable the shift registers with a rate of 6.25 MHz
  SIGNAL valid : std_ulogic;

  -- shift register 1
  SIGNAL d_sr1, q_sr1 : std_ulogic_vector((SR1_LENGTH - 1) DOWNTO 0);

  -- shift register 2
  SIGNAL d_sr2, q_sr2 : std_ulogic_vector((SR2_LENGTH - 1) DOWNTO 0);

  -- bit that is chosen for symbol decision
  SIGNAL symbol_bit : std_ulogic;

  -- signals for restart_o signal (counters, mod values, ...)
  SIGNAL current_state_restart_counter, next_state_restart_counter, mod_value_restart_counter:
    ⇨ unsigned (SR2_LENGTH-1 DOWNTO 0);

BEGIN

  valid_o <= '1' when (current_state_mod8_counter = 0) and (rst_ni = '1') else '0';

  -- modulo 8 counter for valid signal
  current_state_mod8_counter <= (others => '0') when rst_ni = '0' else next_state_mod8_counter
  ⇨ when rising_edge(clk_i);
  next_state_mod8_counter <= (current_state_mod8_counter + 1);
  valid <= '1' when current_state_mod8_counter = 7 else '0';

  -- shift register 1
  q_sr1 <= std_ulogic_vector(to_unsigned(INIT, q_sr1'length)) when rst_ni = '0' else d_sr1 when
  ⇨ rising_edge(clk_i) and valid = '1';

```



```

d_sr1((SR1_LENGTH - 2) DOWNT0 0) <= q_sr1(SR1_LENGTH-1 DOWNT0 1);
d_sr1(SR1_LENGTH-1) <= q_sr1(1) XOR q_sr1(0);

-- shift register 2
q_sr2 <= std_ulogic_vector(to_unsigned(INIT, q_sr2'length)) when rst_ni = '0' else d_sr2 when
↪ rising_edge(clk_i) and valid = '1';
d_sr2((SR2_LENGTH - 2) DOWNT0 0) <= q_sr2(SR2_LENGTH-1 DOWNT0 1);
d_sr2(SR2_LENGTH-1) <= q_sr2(1) XOR q_sr2(0);

-- choose which shift register should be chosen for the symbol decision
symbol_bit <= q_sr1(0) when sel_pn_i = '0' else q_sr2(0);

-- symbol decision
symbol_o <= std_ulogic_vector(to_signed(PLUS1, symbol_o'length)) when symbol_bit = '0' else
↪ std_ulogic_vector(to_signed(MINUS1, symbol_o'length));

-- restart signal
next_state_restart_counter <= (current_state_restart_counter + 1) mod
↪ mod_value_restart_counter;
current_state_restart_counter <= (others => '0') when rst_ni = '0' else
↪ next_state_restart_counter when rising_edge(clk_i) and valid = '1';

mod_value_restart_counter <= to_unsigned(MOD_COUNTER1, mod_value_restart_counter'length) when
↪ sel_pn_i = '0'
                                else to_unsigned(MOD_COUNTER2,
↪ mod_value_restart_counter'length);

restart_o <= '1' when current_state_restart_counter = (mod_value_restart_counter - 1) else '0';

END structure;

```

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;
USE STD.textio.ALL;

ENTITY t_datagen IS

END t_datagen;

ARCHITECTURE tbench OF t_datagen IS

    COMPONENT datagen IS
        GENERIC (
            INIT : integer);
        PORT (
            clk_i      : IN std_ulogic;
            rst_ni     : IN std_ulogic;
            sel_pn_i   : IN std_ulogic;
            restart_o  : OUT std_ulogic;
            valid_o    : OUT std_ulogic;
            symbol_o   : OUT std_ulogic_vector(7 DOWNT0 0));
    END COMPONENT datagen;

    -- component ports
    SIGNAL clk      : std_ulogic;
    SIGNAL rst_n    : std_ulogic;
    SIGNAL valid    : std_ulogic;
    SIGNAL symbol   : std_ulogic_vector(7 DOWNT0 0);

```

```

-- definition of a clock period
CONSTANT period : time := 20 ns;
-- switch for clock generator
SIGNAL clken_p : boolean := true;

BEGIN

-- component instantiation
DUT : datagen
  GENERIC MAP (
    INIT => 12582912) -- OBS! some initial value is required here
  PORT MAP (
    clk_i    => clk,
    rst_ni   => rst_n,
    sel_pn_i => '1',
    restart_o => OPEN,
    valid_o  => valid,
    symbol_o  => symbol);

-- clock generation
clock_proc : PROCESS
BEGIN
  WHILE clken_p LOOP
    clk <= '0'; WAIT FOR period/2;
    clk <= '1'; WAIT FOR period/2;
  END LOOP;
  WAIT;
END PROCESS;

reset : rst_n <= '0', '1' AFTER period;

observer : PROCESS
  VARIABLE Lo : line; -- pointer to file output buffer
  VARIABLE Vo : integer;
  FILE resultfile : text OPEN write_mode IS "log/datagen_result.dat";
BEGIN

  WAIT UNTIL rst_n = '1'; -- wait for reset

  FOR k IN 0 TO 4*10**3-1 LOOP
    WAIT UNTIL clk = '1';
    IF valid = '1' THEN
      Vo := to_integer(signed(symbol));
      write(Lo, Vo);
      writeline(resultfile, Lo);
    END IF;
  END LOOP;

  clken_p <= false; -- switch off clock generator

  WAIT;
END PROCESS;
END tbench;

```